

Sensor de distância média

Sensor: SHARP GP2Y0A21YK0F



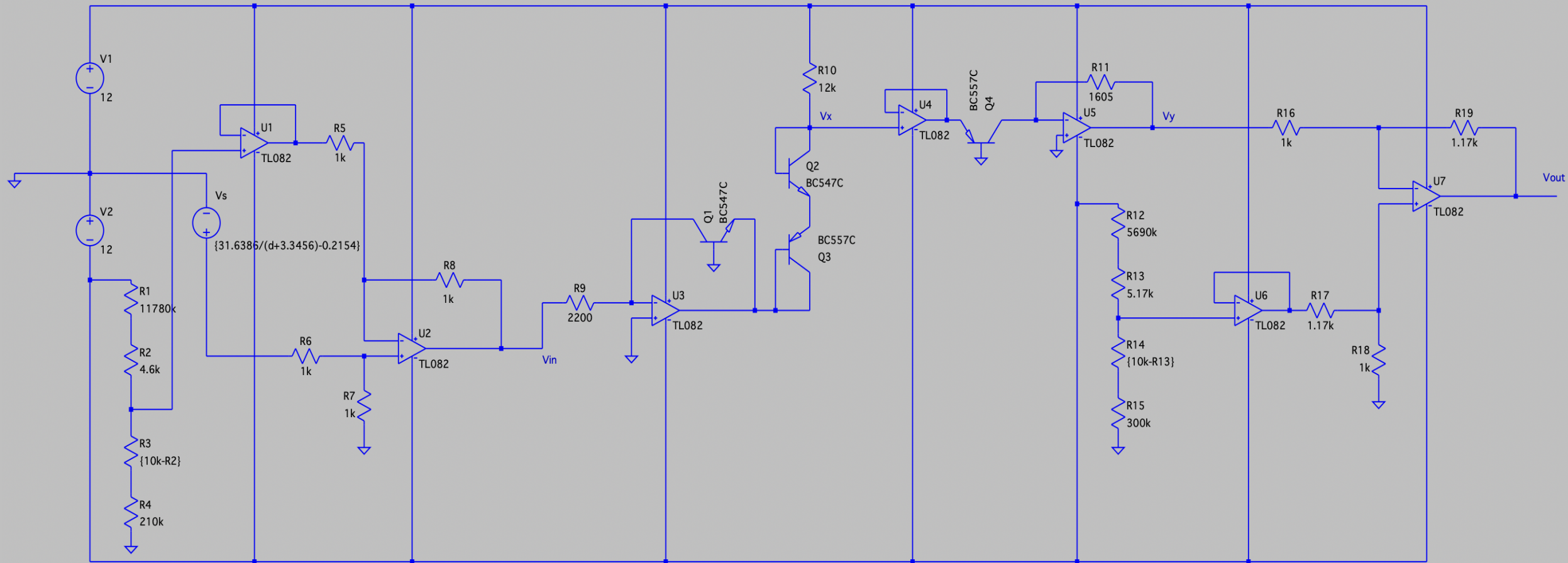


Diagrama de Blocos

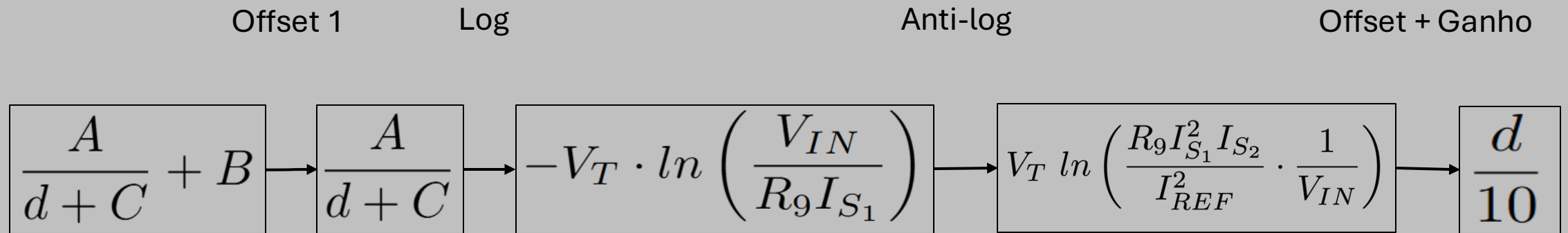


$$V_{IN} = \frac{A}{d + C}$$

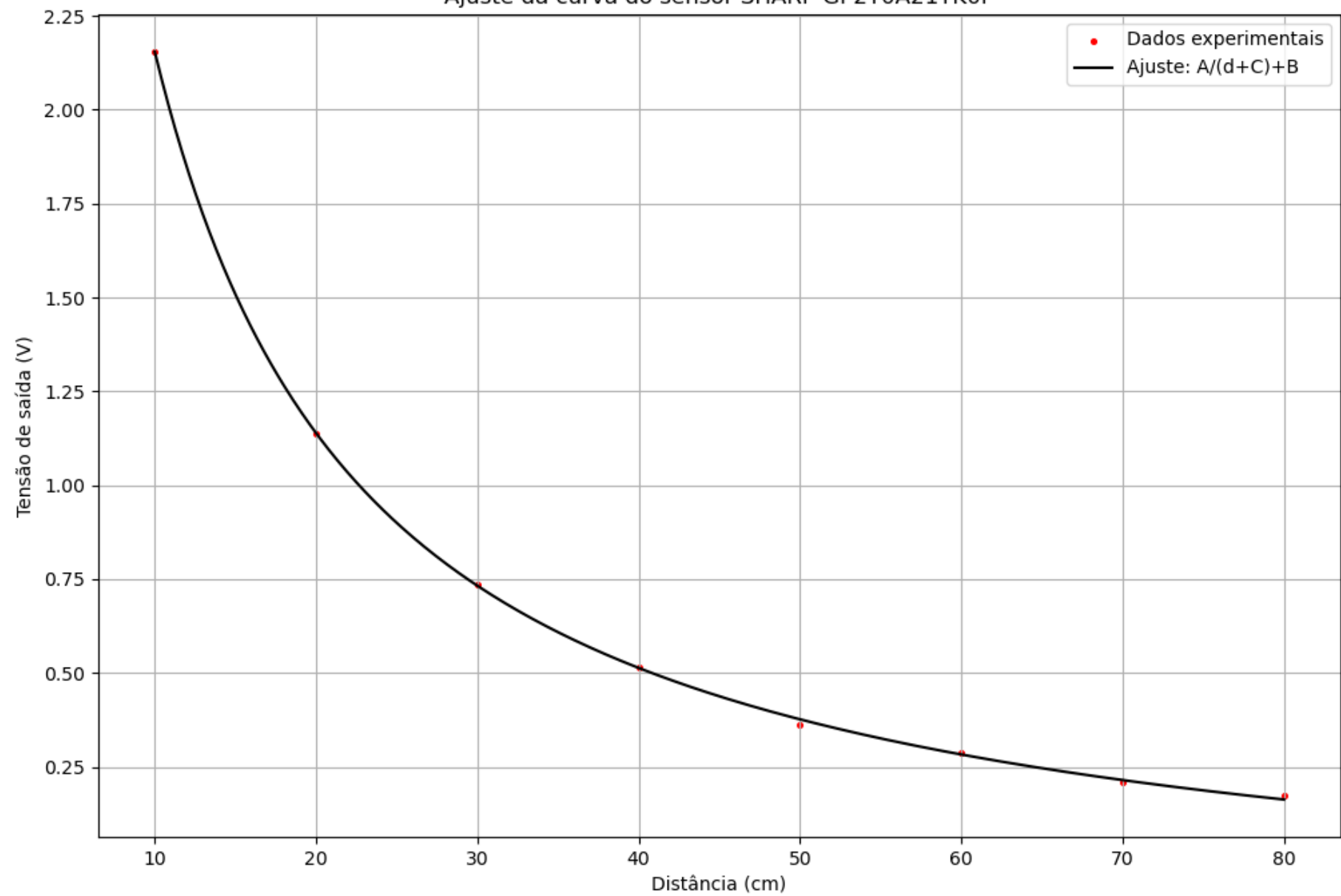
Ajuste da curva do sensor SHARP GP2Y0A21YK0F



Circuito subtrator

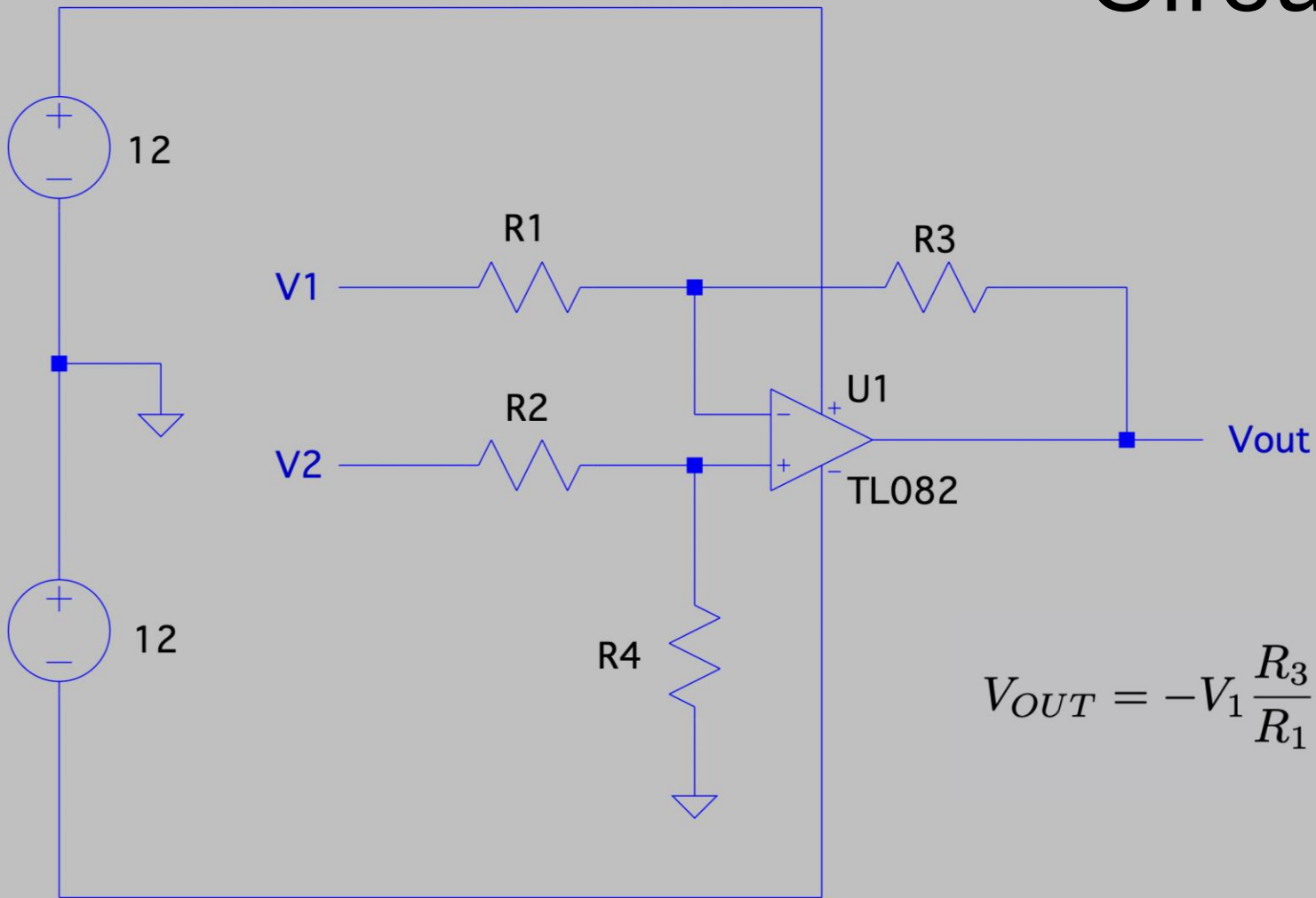
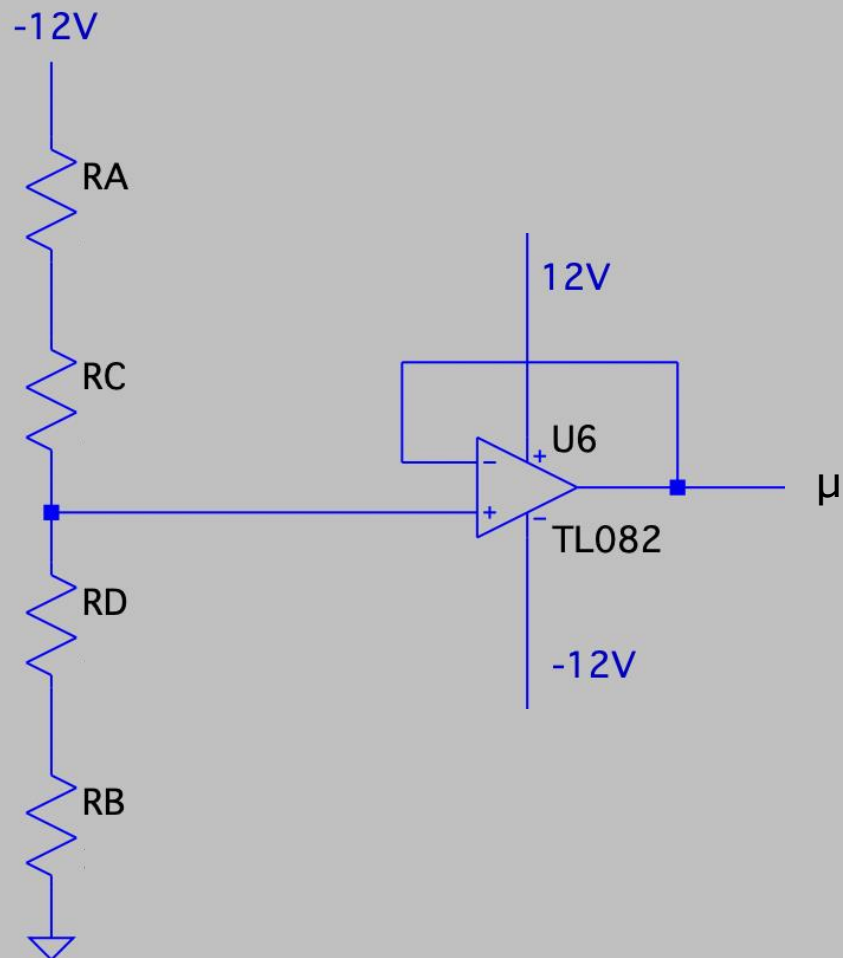
$$V_{OUT} = -V_1 \frac{R_3}{R_1} + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$




$$R_A = \frac{10k}{2} \left(\frac{12 + \mu}{\Delta} - 1 \right)$$

$$R_B = \frac{10k}{2} \left(-\frac{\mu}{\Delta} - 1 \right)$$

$$R_D = 10k - R_C$$

Log e Anti-log

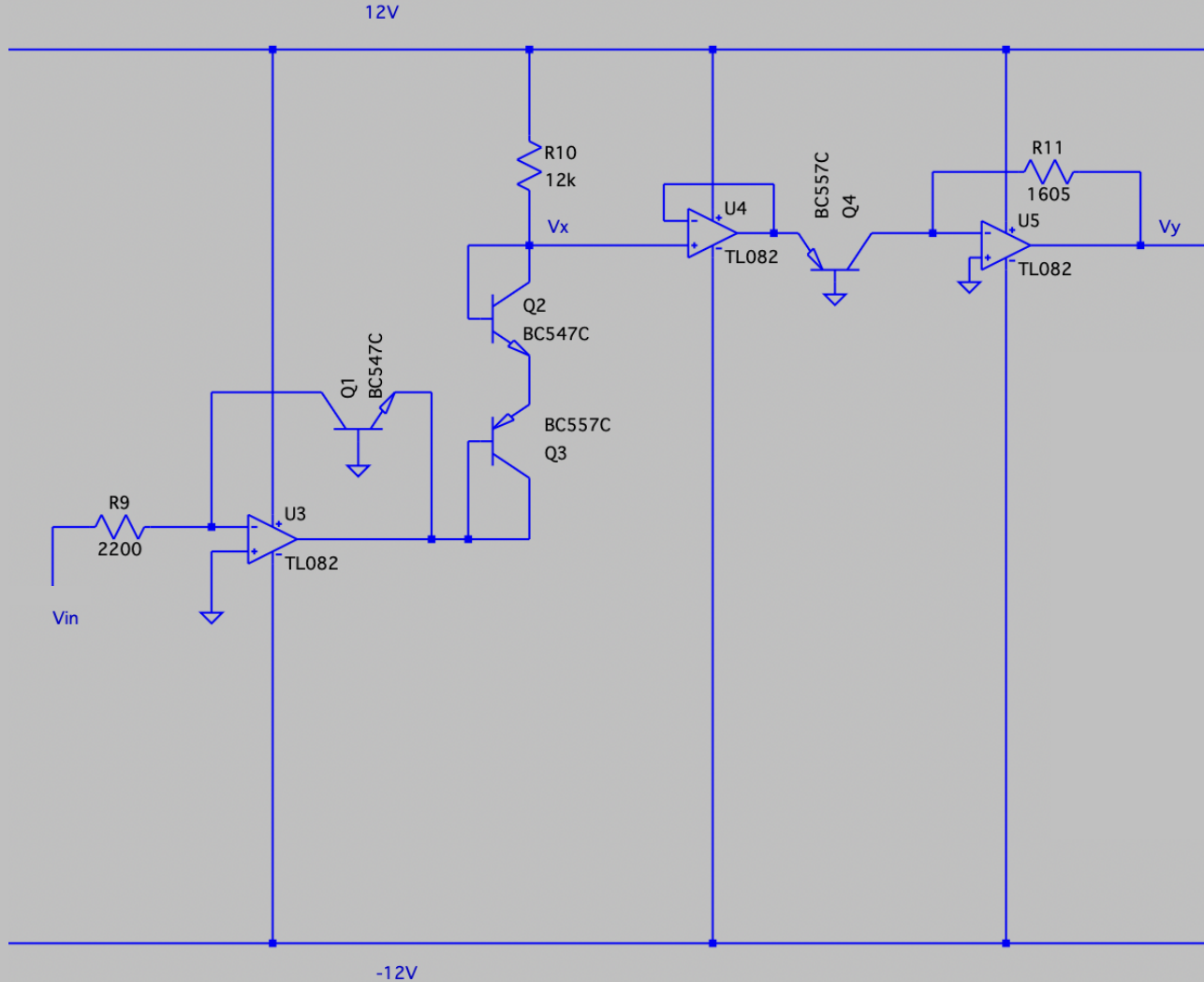

$$V_{BE_1} = V_T \cdot \ln \left(\frac{I_{C_1}}{I_{S_1}} \right), \quad I_{C_1} = \frac{V_{IN}}{R_9}$$

$$V_{BE_1} = V_T \cdot \ln \left(\frac{V_{IN}}{R_9 I_{S_1}} \right)$$

$$V_{E_1} = V_{B_1} - V_{BE_1} = 0 - V_T \cdot \ln \left(\frac{V_{IN}}{R_9 I_{S_1}} \right) = -V_T \cdot \ln \left(\frac{V_{IN}}{R_9 I_{S_1}} \right)$$

$$V_{BE_2} = V_T \cdot \ln \left(\frac{I_{REF}}{I_{S_1}} \right)$$

$$V_{BE_3} = V_T \cdot \ln \left(\frac{I_{REF}}{I_{S_2}} \right)$$

tomando,

$$V_{IN} = \frac{A}{x}, \quad x = d + C$$

em que d é a distância e $V_{SENSOR} = V_{IN} + B$

$$V_X = V_{E_1} + V_{E_3} + V_{E_2} = V_T \left(-\ln \left(\frac{A}{x R_9 I_{S_1}} \right) + \ln \left(\frac{I_{REF}}{I_{S_2}} \right) + \ln \left(\frac{I_{REF}}{I_{S_1}} \right) \right)$$


$$I_{C_2} = I_{S_2} e^{\frac{V_{E_2}}{V_T}}$$


$$I_{C_2} = I_{S_2} \exp \left(\frac{V_T \left(-\ln \left(\frac{A}{x R_9 I_{S_1}} \right) + \ln \left(\frac{I_{REF}}{I_{S_2}} \right) + \ln \left(\frac{I_{REF}}{I_{S_1}} \right) \right)}{V_T} \right)$$

$$I_{C_2} = \frac{R_9 I_{REF}^2}{A} x, \quad I_{REF} = \frac{12 - V_X}{R_{10}}$$


$$I_{C_2} = \frac{R_9 (12 - V_X)^2}{A R_{10}^2} x$$
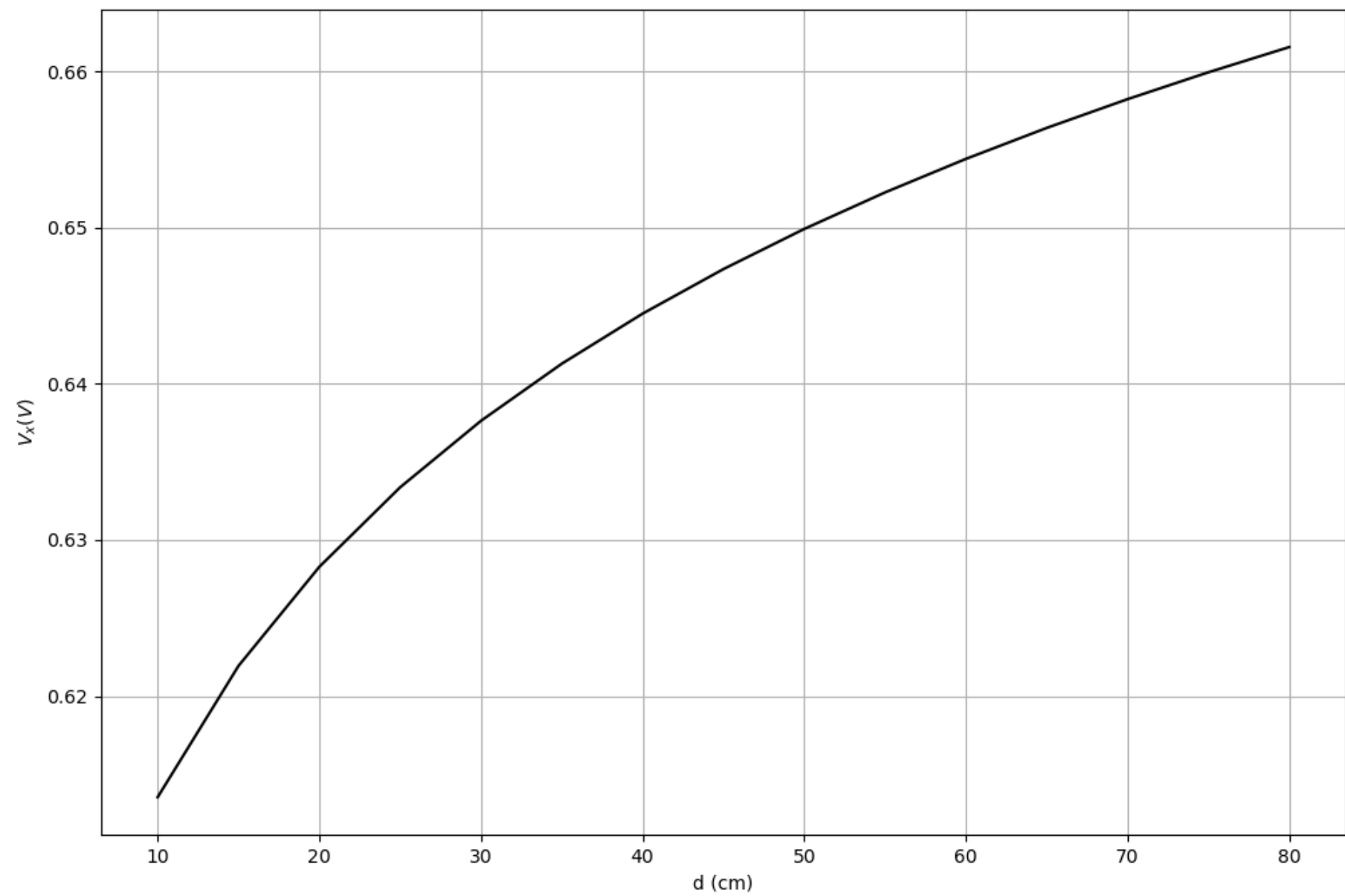
$$V_Y = -I_{C_2} R_{11} = -\frac{R_9 R_{11} (12 - V_X)^2}{A R_{10}^2} x$$



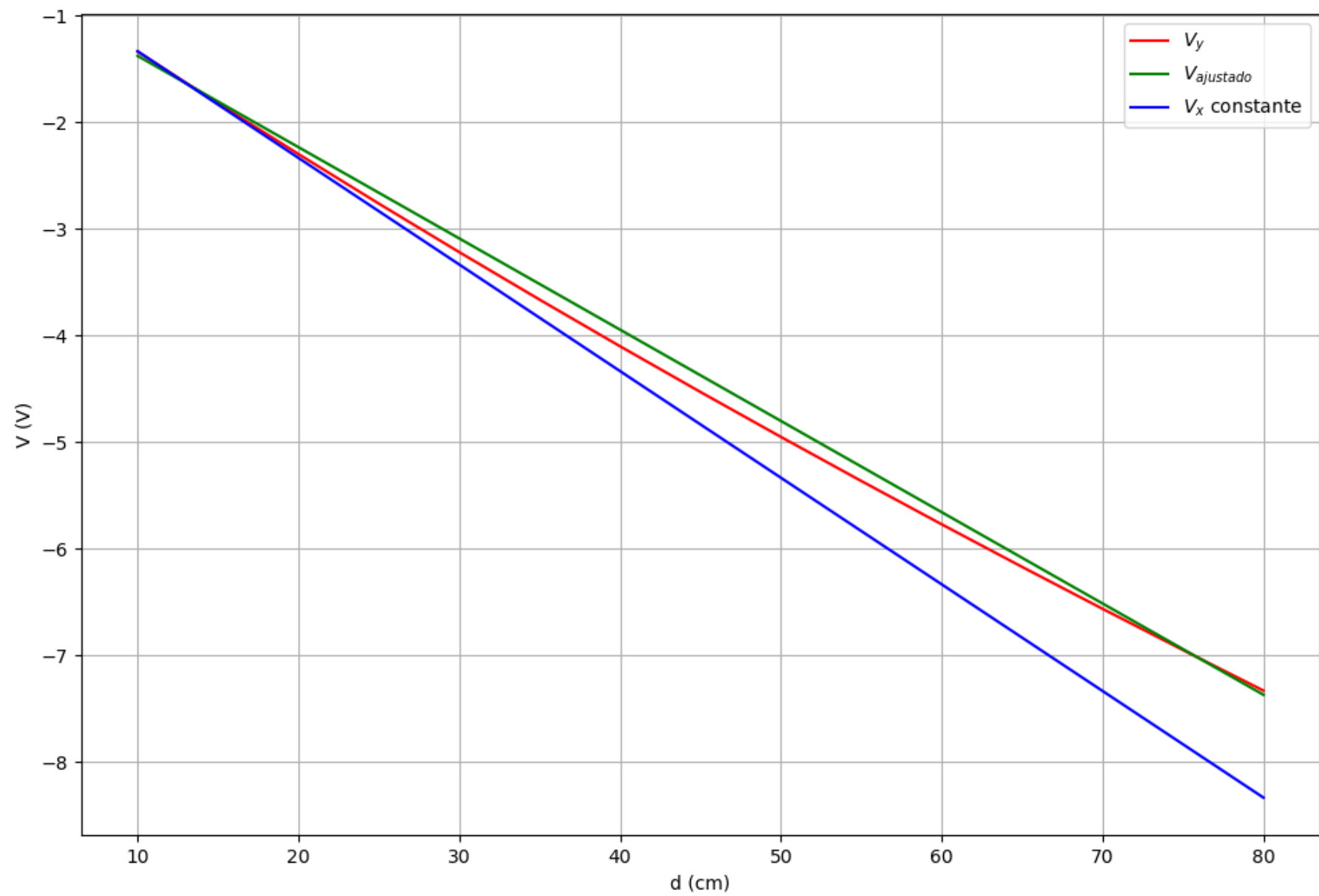

Circuito subtrator

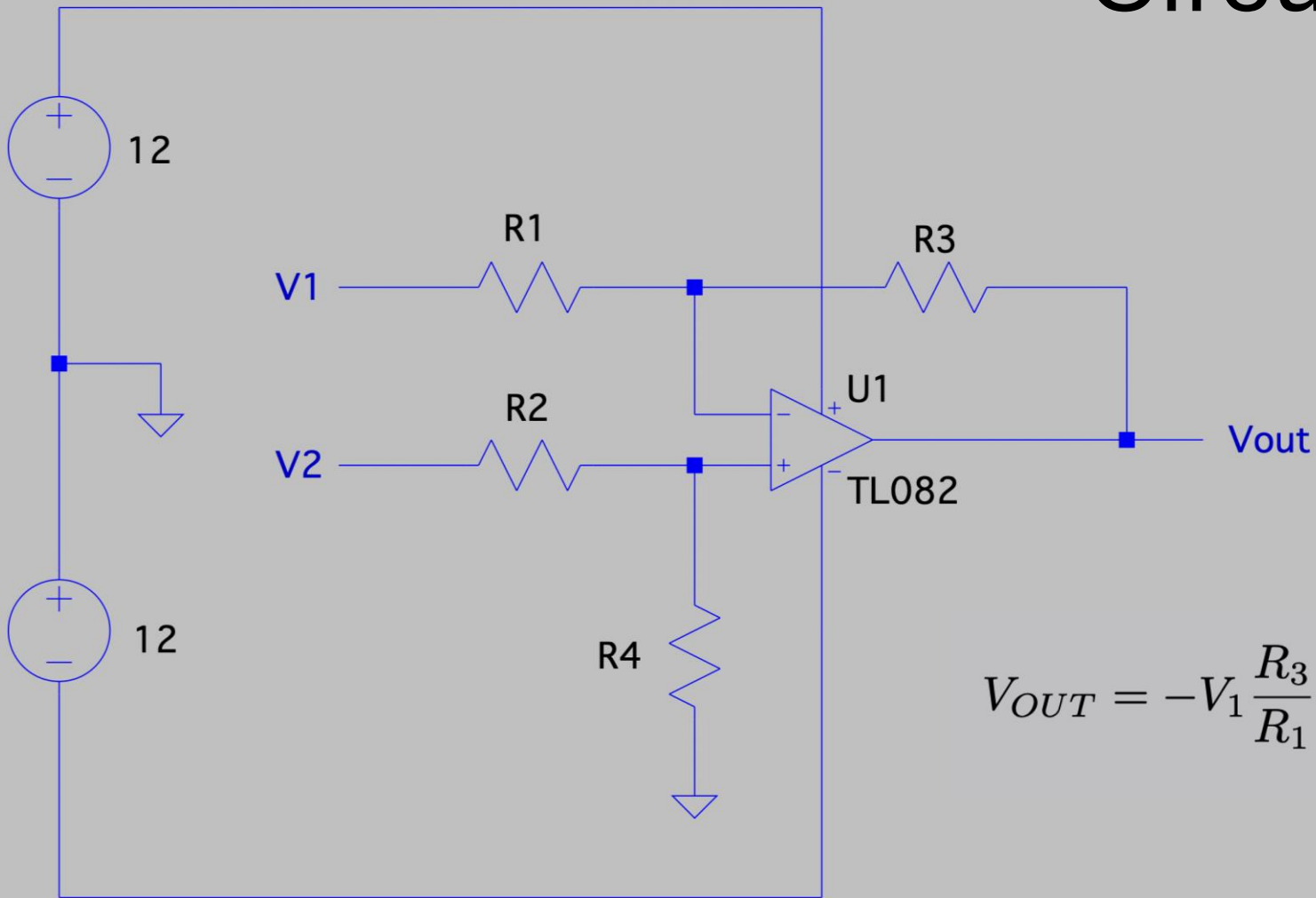

$$V_{OUT} = -V_1 \frac{R_3}{R_1} + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

